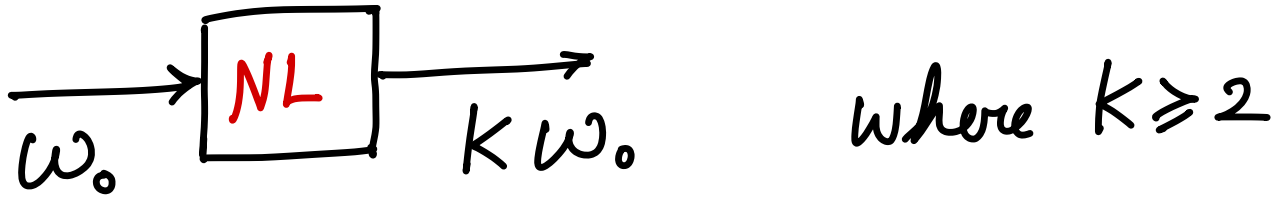





Frequency Multipliers




> LTI cannot work.

- Nonlinear element ✓
- Time variation.

Non-linear multiplier

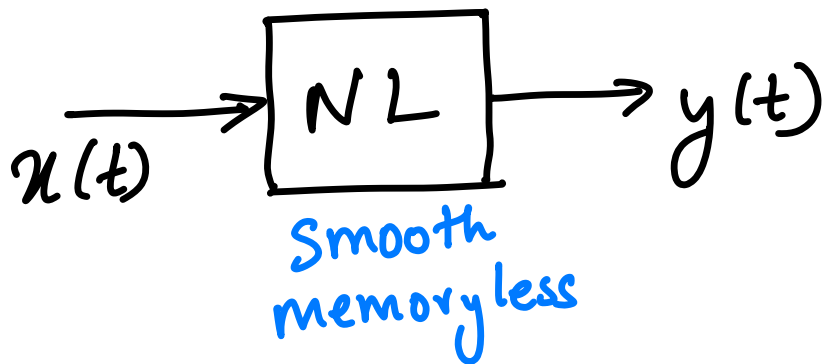
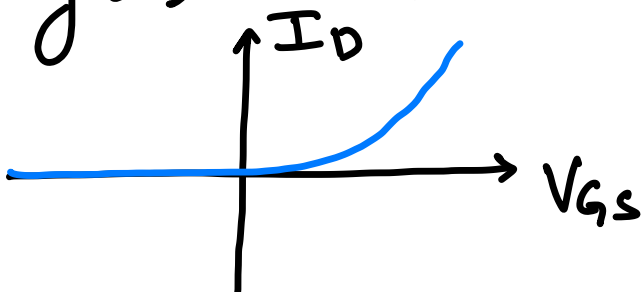
$$y(t) = a_0 + a_1 x(t) + a_2 x^2(t) + \dots$$



$$x(t) = A \cos(\omega_0 t)$$

$$y(t) = a_0 + a_1 A \cos(\omega_0 t) + a_2 A^2 \cos^2(\omega_0 t) + \dots$$

$$\Rightarrow y(t) = b_0 + b_1 \cos(\omega_0 t) + b_2 \cos(2\omega_0 t) + \dots$$

$$b_0 = a_0 + \frac{a_2 A^2}{2} + \frac{3a_4 A^4}{8} + \dots$$

$$b_1 = a_1 A + \frac{3a_3 A^3}{4} + \dots$$

$$b_2 = \frac{a_2 A^2}{2} + \frac{a_4 A^4}{2} + \dots$$

$$b_3 = \frac{a_3 A^3}{4} + \dots$$

> $a_x \rightarrow$ Taylor/Polynomial Coeff.


$b_x \rightarrow$ Harmonic coeffs.

> Leading term in b_x is $a_x A^x$.

> Even order $b_x \leftrightarrow$ Even order a_x .



$$G_{C,K} \triangleq \frac{P_{out}(K\omega_0)}{P_{in}(\omega_0)} \cdot \eta \quad \eta = G_{C,K} > 1 \Rightarrow \text{Active.}$$

System/Circuit Level View


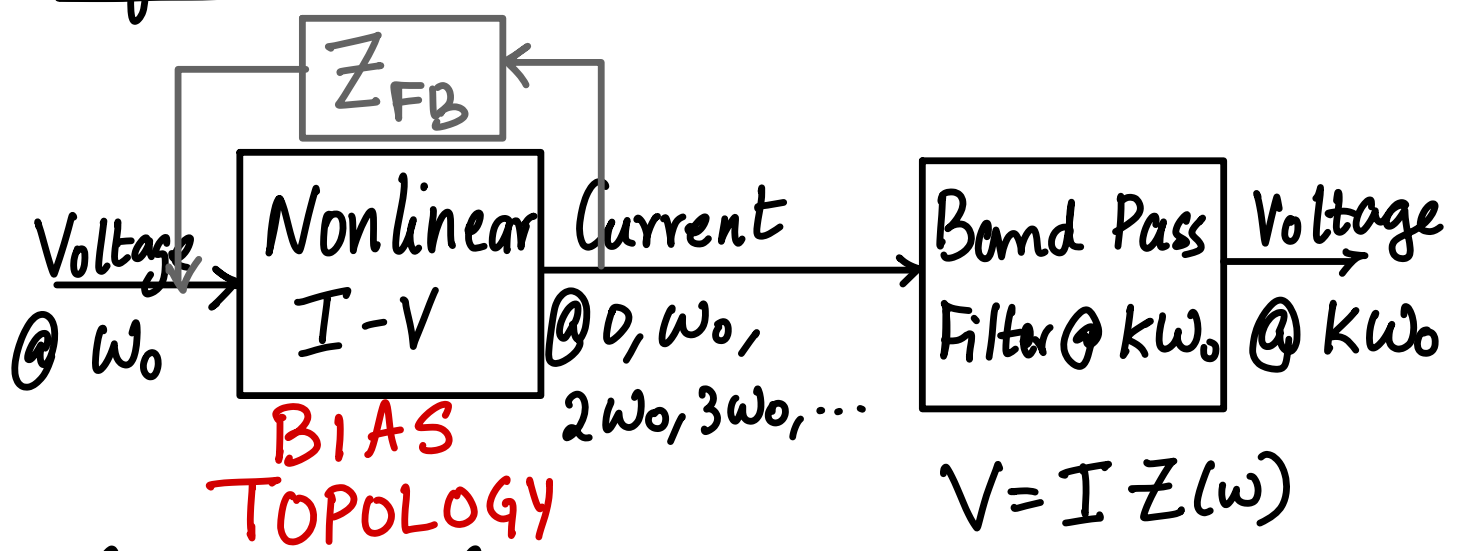


Circuit Implementation

Diode

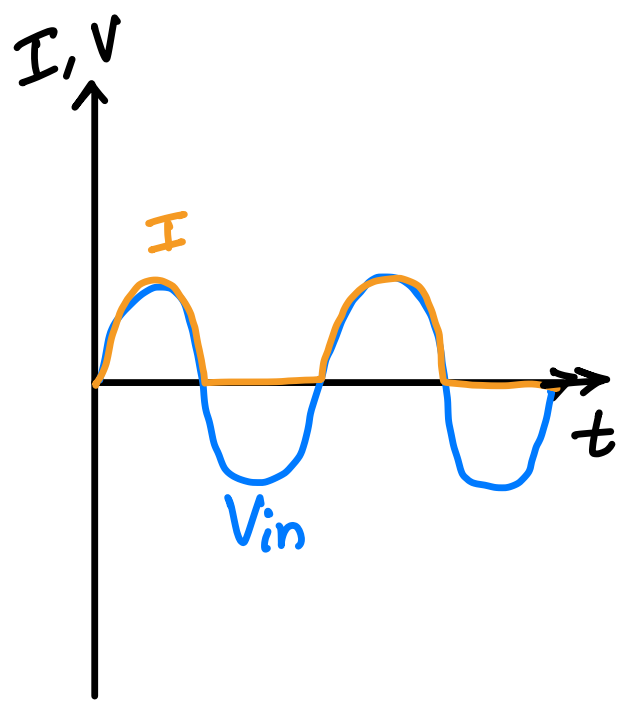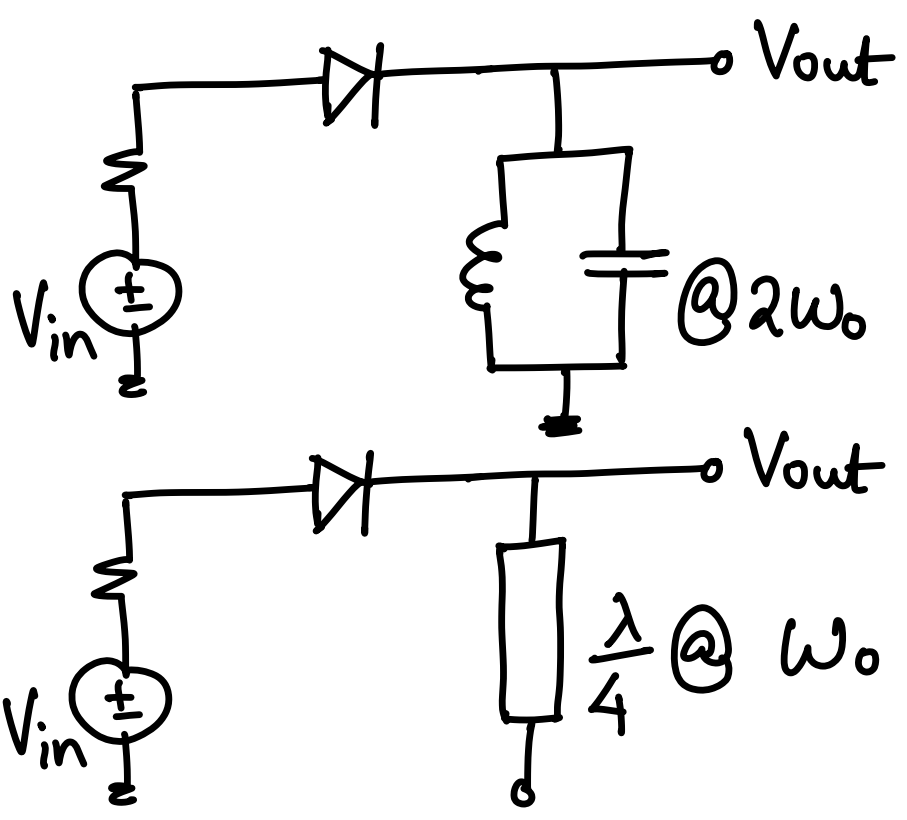


Transistor

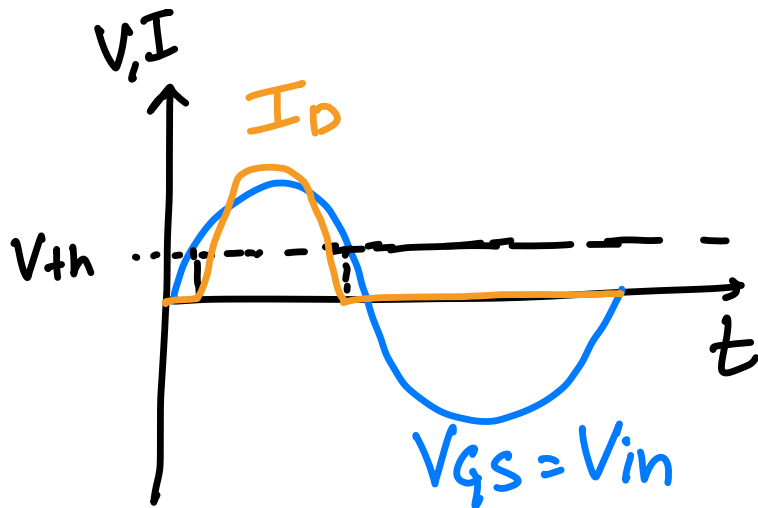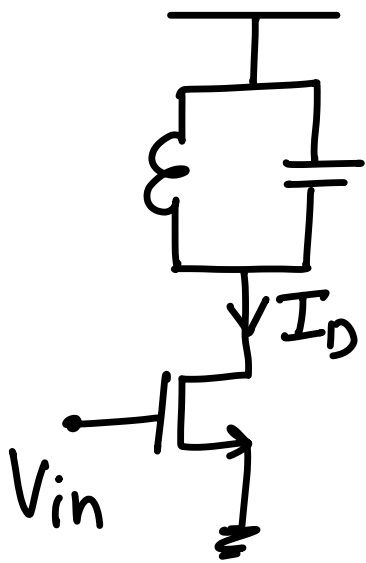

BIAS POINT SELECTION

> Given a NL IV device, what should be the bias to maximize power at $K\omega_0$.


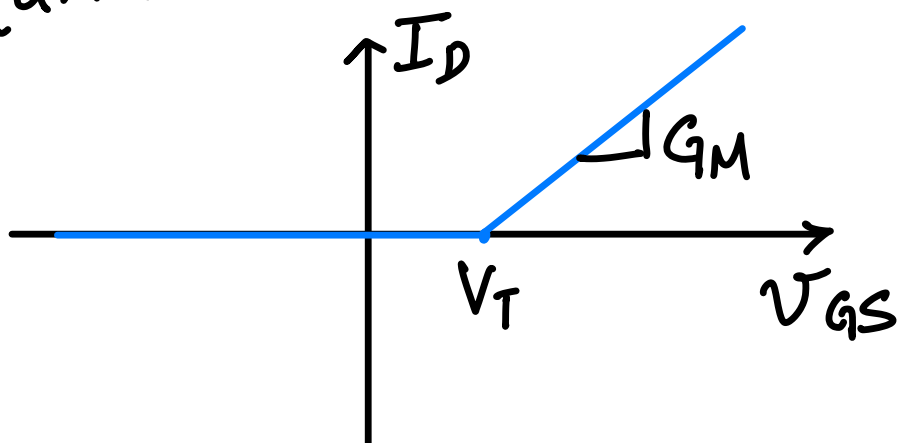
Assumption: IV is Piecewise linear
(aka Truncated Cosine Model)



> Good model for short channel FETs.

$$I_D = \begin{cases} g_m (V_{GS} - V_T) & V_{GS} \geq V_T \\ 0 & V_{GS} < V_T \end{cases}$$
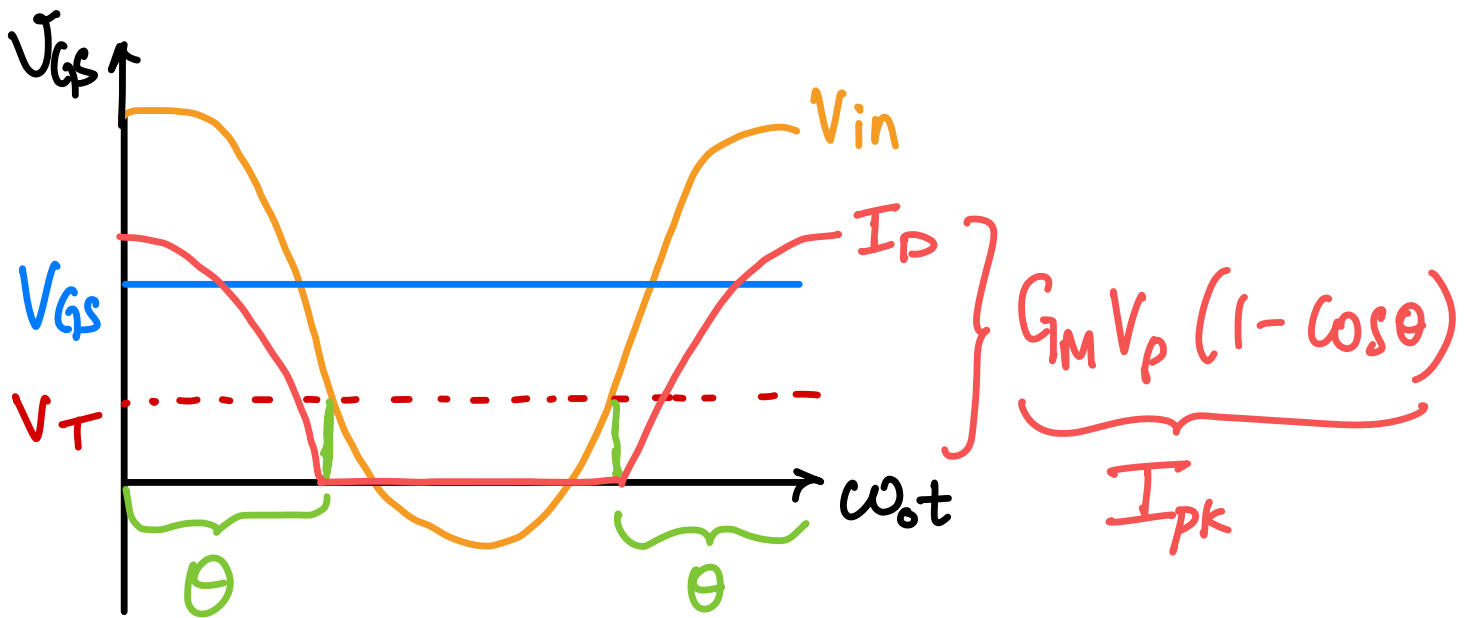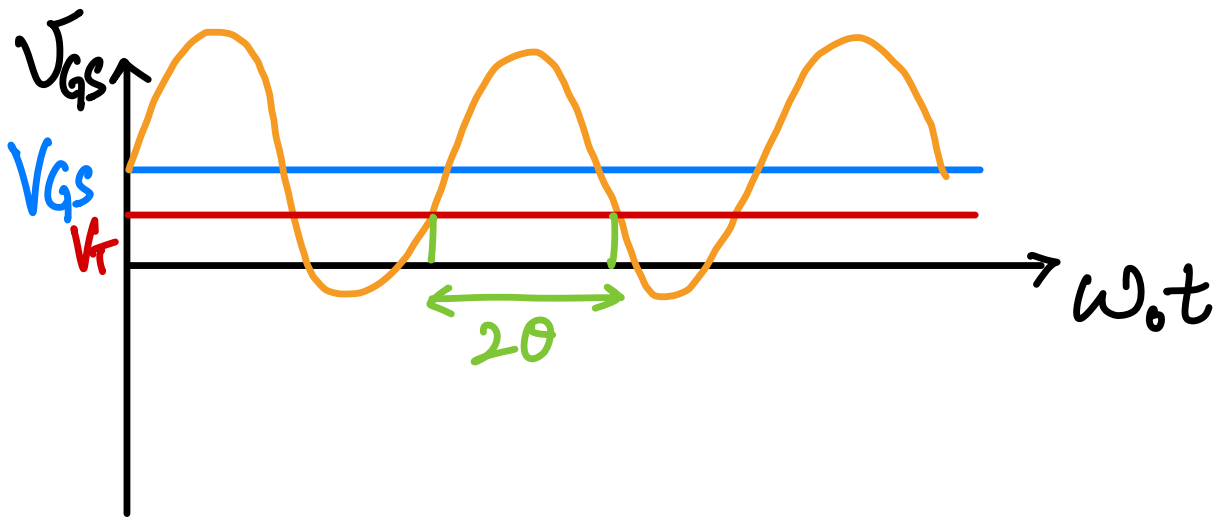
$$V_{GS} = V_{GS} + V_p \cos(\omega_0 t)$$



$2\theta \rightarrow$ Conduction Angle.

$$V_{GS} + V_p \cos\theta = V_T$$

$$\cos\theta = \frac{V_T - V_{GS}}{V_P}$$

θ depends on both V_{GS} & V_P .


$$I_D = G_M (V_{GS} - V_T) \quad V_{GS} > V_T$$

$$= G_M (V_{GS} - V_T + V_P \cos(\omega_0 t))$$

$$= G_M (-V_P \cos\theta + V_P \cos(\omega_0 t))$$

$$I_D = \begin{cases} G_M V_P (\cos(\omega_0 t) - \cos\theta) & |\omega_0 t| < \theta \\ 0 & |\omega_0 t| > \theta \end{cases}$$

$$I_{pk} = G_M V_P (1 - \cos\theta)$$

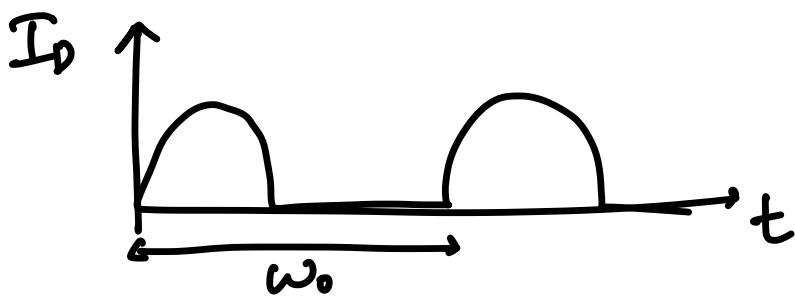

$$I_D(t) = I_0 + \sum_{n=1}^{\infty} I_n \cos(n\omega_0 t)$$

$$I_0 = \frac{G_m V_p}{2\pi} (2 \sin\theta - 2\theta \cos\theta)$$


$$I_1 = \frac{G_m V_p}{2\pi} (2\theta - \sin(2\theta))$$

$$I_N = \frac{G_m V_p}{\pi} \left[\frac{2 \{ \sin(N\theta) \cos\theta - N \cos(N\theta) \sin\theta \}}{N(N^2-1)} \right]$$

$N \geq 2$

$$\alpha_N(\theta) = \frac{I_N(\theta)}{I_{pk}}$$

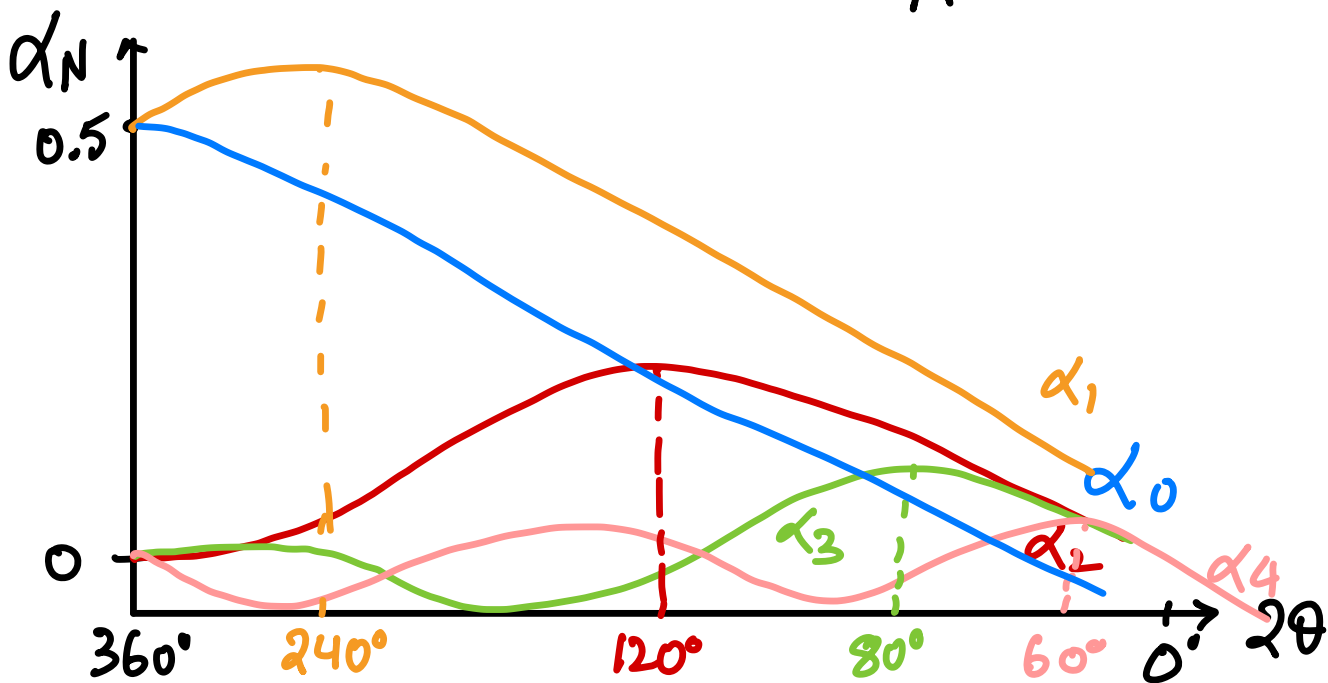→ Measures how much power goes into N^{th} harmonic.




$$2\theta_{opt} \approx \frac{240^\circ}{N}$$

Optimal Conduction Angle.

$$\frac{d_N}{d_0} = \frac{I_N}{I_0}$$

At optimum, this is almost constant.

$$\eta_{opt} \approx 63\%$$

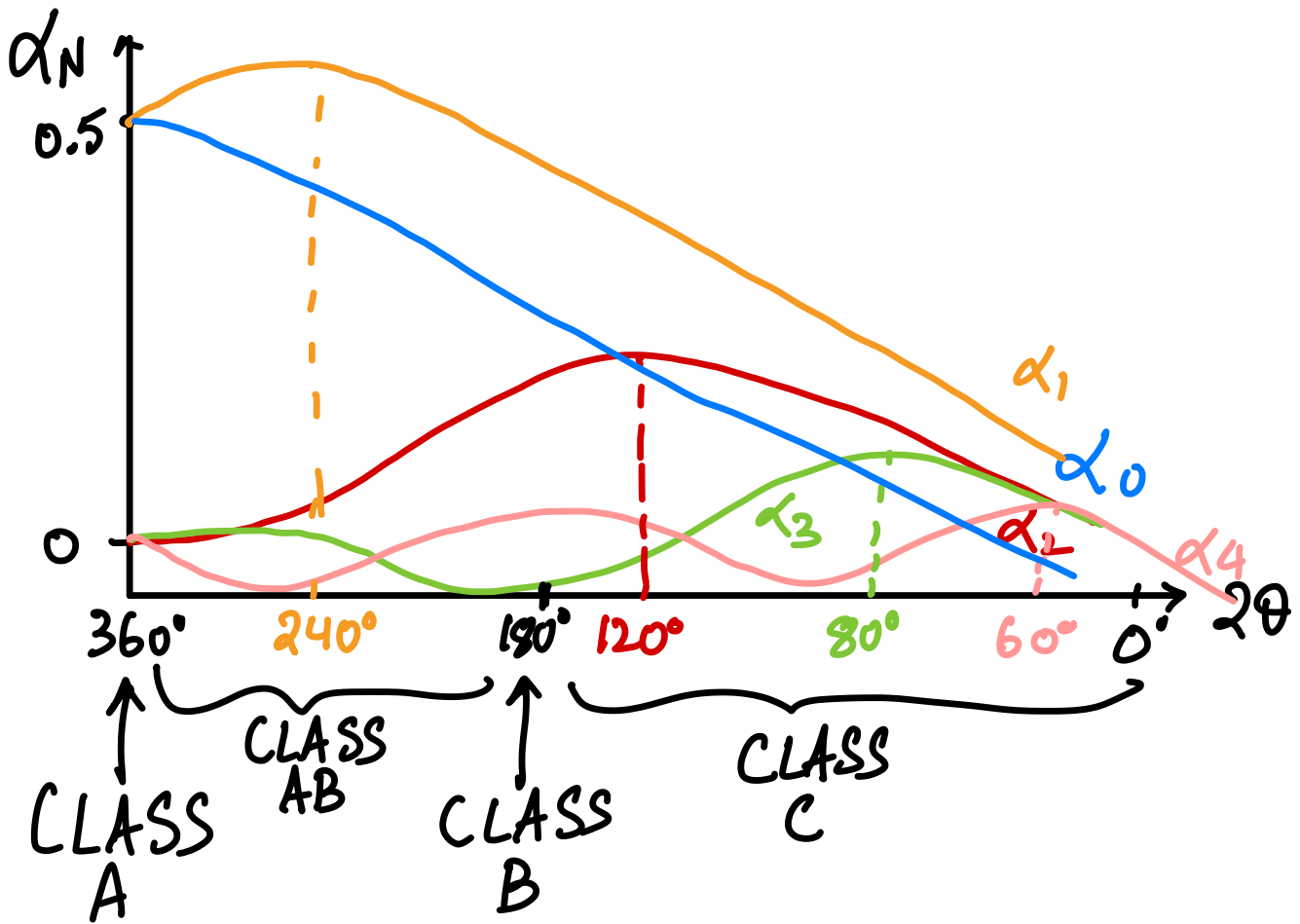

Caution: This is valid under the truncated cosine model.

Doubler x2 vs Quadrupler

$$I_2(\theta_{opt}) = G_m V_p (0.1378)$$

$$I_4(\theta_{opt}) = G_m V_p (0.01857)$$

$$V_{p2} = G_m V_p (0.1378) R_{out}$$

$$I_{2x2}(\theta_{opt}^{2x2}) = G_m^2 V_p [0.1378^2] R_{out}$$

$$\frac{I_{2x2}(\theta_{opt}^{2x2})}{2x2} = G_m V_p [0.0189] A_v$$

$$I_4(\theta_{opt}^4) = G_m V_p [0.01857].$$

Caveats

> Truncated Cosine Assumption. Waveform Shaping to beat this.

> If you can amplify $\boxed{x2} \rightarrow \boxed{x2}$ is better.

Takeaways

- > RF frequencies (100 GHz & below)
Cascaded doublers are better.
- > THz frequencies (Above 100 GHz),
Quadruplers are better.
- > Waveform engineering/shaping changes this dogma.


TOPOLOGY SELECTION

Balanced Multipliers

$$y_p(t) = f(x(t)) = b_0 + b_1 \cos(\omega_0 t) + b_2 \cos^2(\omega_0 t) + \dots$$

$$y_n(t) = f(-x(t)) = b_0 - b_1 \cos(\omega_0 t) + b_2 \cos^2(\omega_0 t) - b_3 \cos^3(\omega_0 t) + \dots$$
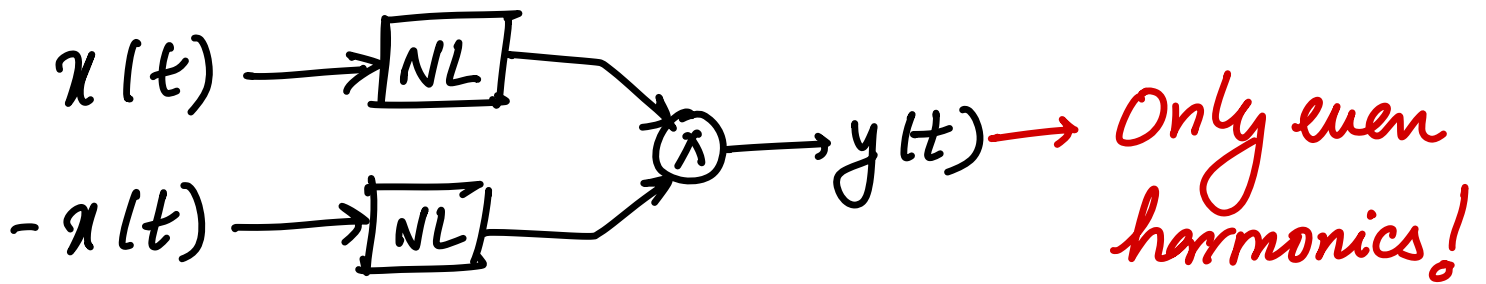
$$y_p(t) + y_n(t) = 2 \left[b_0 + b_2 \cos^2(2\omega_0 t) + b_4 \cos^4(2\omega_0 t) + \dots \right]$$



Intuitive Viewpoint

$$\cos(\omega_0 t) + \cos(\omega_0 t + 180^\circ) = 0$$


$$\downarrow 2x \qquad \qquad \qquad \downarrow 2x$$

$$\cos(2\omega_0 t) + \cos(2\omega_0 t) = 2\cos(2\omega_0 t)$$



3x

$$\cos(3\omega_0 t) + \cos(3\omega_0 t + 180^\circ) = 0$$

PHASOR

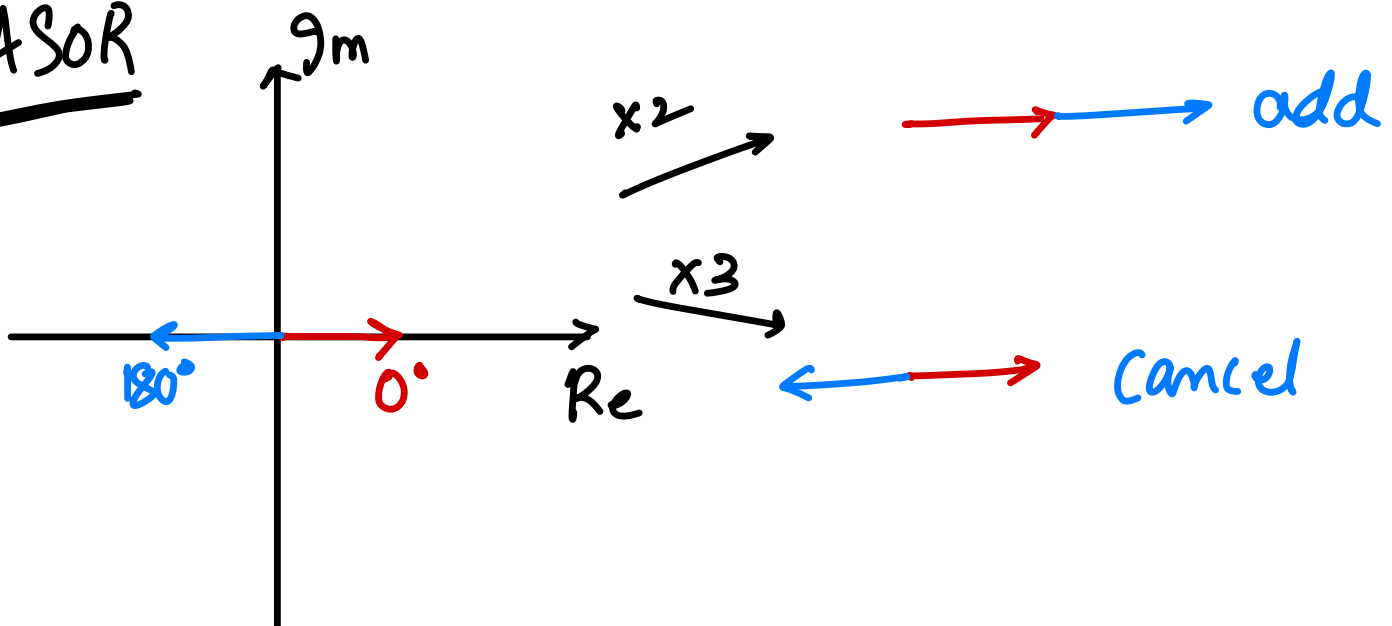

Tripler \Rightarrow Three Phase Signals.

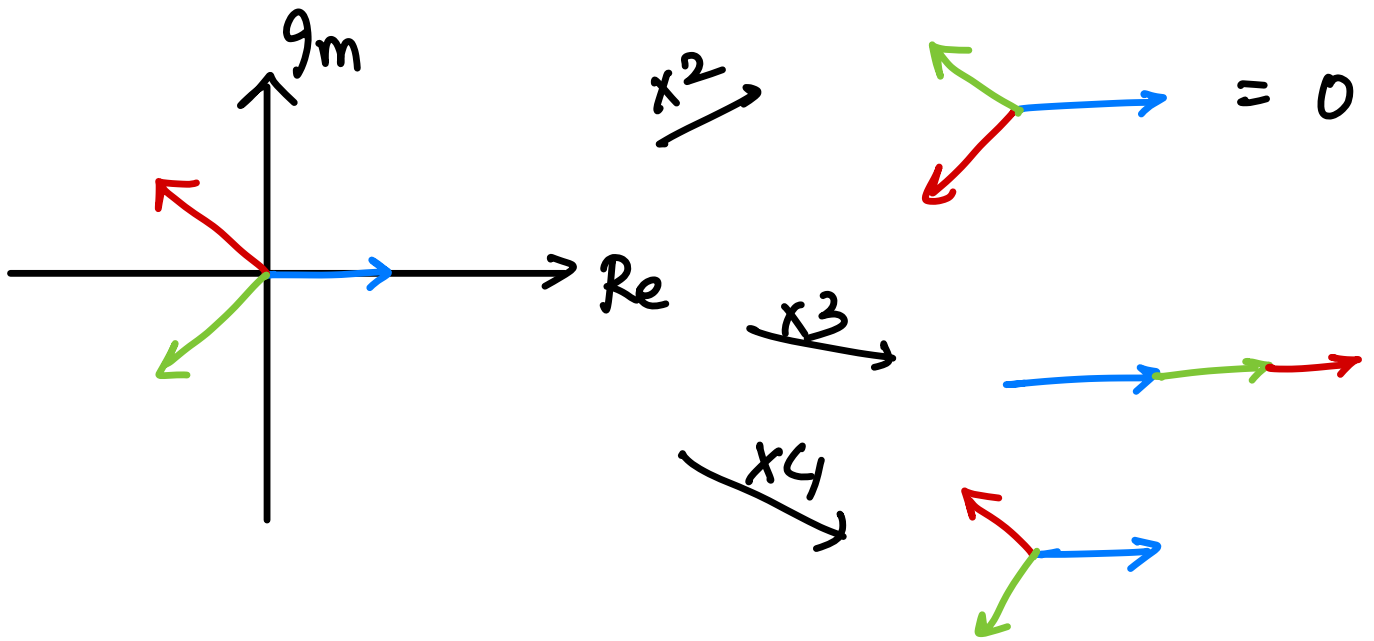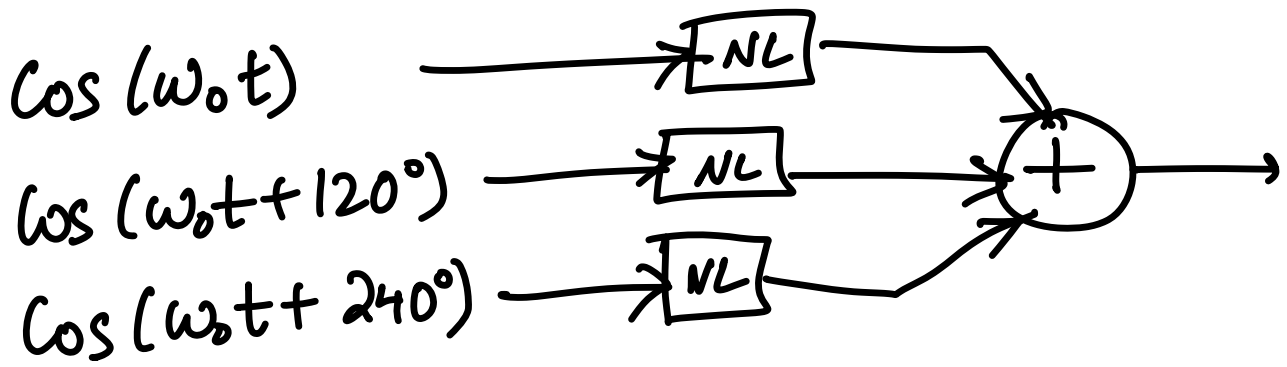

Circuit Implementation

Diodes

